

Vol. 15, No. 12

December 1996

U.S. \$3.95
Can. \$6.25



Monitoring Times[®]

Your Personal
Communications Source

Printed in the United States

Scanning
Washington D.C.
and the

INAUGURATION

lowpowerradio.blogspot.com



teurs to use their FCC-assigned call signs.

With regard to the 550-1600 kHz MF band, the greatest distance I have achieved for a reliable signal was 1/4 to 1/2 mile while monitoring the signal via my car radio. The tests were conducted with a 10-foot vertical transmitting antenna, in combination with four 60-foot radials and an impedance-matching network at the antenna feed point.

■ Signal Quality

The short antennas permitted for use under Part 15 of the rules are extremely narrow in 2:1 SWR bandwidth. My antenna had a bandwidth of only 3 kHz. This means that AM transmissions are limited in fidelity by the narrow-band response of the antenna. So, don't expect high signal quality if you transmit music. Single-tone audio and voice modulation is not impaired significantly.

■ A Practical Transmitter

Figure 1 shows a simple AM transmitter you can build for a modest outlay of money. Five low-cost transistors are used to create an RF section and a modulator. This transmitter is designed for use from 1400 to 1600 kHz or lower. It is well within the lawful power limit specified for the MF range.

Q1 operates as a self-excited oscillator. Crystal control could be used, but crystals are expensive. C1 is adjusted for the desired operating frequency. Select a frequency that falls between existing BC band signals.

Q2 amplifies the oscillator output signal, which is then routed to the final RF amplifier, Q3. T1 is a tuned circuit that matches the Q3 collector to a 10-foot antenna. C2 is used to resonate the tuned circuit.

Q4 operates as a mic or audio amplifier. Modulation is accomplished by means of Q5. A transistor radio audio output transformer is used as the modulation transformer. A 1000-ohm center-tapped transformer that is designed for use with an 8-ohm speaker is suitable. The output winding is not used. Audio gain control R1 sets the modulation percentage.

D1 allows Q2 to receive modulated dc voltage, but permits only the positive audio peaks to reach the collector of Q3. This ensures that upward modulation occurs (signal increase with modulation). Negative-going audio peaks would reverse-bias Q3 and cause downward modulation (reduced output power during negative-going audio peaks).

■ Construction

The Figure 1 circuit can be assembled on perf board, or you may use point-to-point

wiring between insulating terminal strips. Keep all RF leads as short and direct as practicable. Q1, Q2 and Q3 should be arranged in a straight line in order to keep them sufficiently isolated from one another. This will help to prevent unwanted self-oscillation of Q2 or Q3. Most of the parts for this project are available from Mouser Electronics.² Amidon toroids are used for L1, L2, L3, L4 and T1.³

■ Operation and Use

The 10-foot antenna wire is connected directly to the junction of C3 and L4 (Figure 1). Look for a clear frequency between 1400 and 1600 kHz and adjust C1 until you hear the transmitter signal on an BC-band radio. Now, adjust C3 for maximum signal strength. A radio with an S meter is best for this purpose.

Connect a microphone or tape player to Q4. Adjust R1 for a setting that produces a transmitted signal which is loud, but not distorted or fuzzy. Operation below 1400 kHz is possible if you add capacitance in parallel with C2. Using a trimmer at with greater maximum capacitance at C1 will also lower the operating frequency.

If you aren't interested in operating this transmitter as a beacon for others to monitor, consider employing it for on-the-air code practice with a friend in your neighborhood. A keyed audio oscillator (500 to 1000 Hz tone) may be connected to J1 for this purpose. Two of these transmitters may be used as part of an intercom system between the house and the workshop if two BC-band radios are included. For intercom use tune one transmitter to, say, 555 kHz and the other to 1600 kHz. This will allow you to communicate without muting the receivers.

You can transmit music from your hi-fi system to a remote site, such as your workshop, deck, or a Walkman AM/FM radio. The possibilities are many.

Building, testing and operating this transmitter can be educational as well as entertaining. Who knows? You may become an MF band DX titan if you operate the Figure 1 circuit as a beacon transmitter!

■ Notes

1 — *The Low-Frequency Scrapbook* was written for experimenters who build equipment and operate in the LF and MF bands under Part 15 of the FCC rules. Contact author Ken Cornell, W2IMB, 225 Baltimore Ave., Pt. Pleasant, NJ 08742.

2 — Amidon Assoc., Inc., 3122 Alpine Ave., Santa Ana, CA 92704. Phone: (714) 850-4660 for parts or a catalog.

3 — Mouser Electronics, 958 N. Main St., Mansfield, TX 76063-4422. Phone: (800) 346-6873 for parts or a catalog.

The professional weather station for people who care about the weather.



Connects to Packet Radiol

Davis Instruments has a complete line of weather stations affordable enough for home and hobby use. Connect the station to packet radio using shareware program available on Davis' BBS.

Features Include:

- Inside & Outside Temps
- Wind Speed & Direction
- Barometer
- Time & Date
- Inside Humidity
- Wind Chill
- Alarms
- Highs & Lows
- Rainfall Option
- Instant Metric Conversion
- Outside Hum. & Dew Point Option
- Optional PC Interface

1-800-678-3669
or visit us at www.davisnet.com

M-F 7 a.m. to 5:30 p.m. Pacific Time • MT672E
FAX 1-510-670-0589 • M/C and VISA
One-year warranty • 30-day money-back guarantee

DAVIS INSTRUMENTS
3465 Diablo Ave., Hayward, CA 94545

ACTIVE PRESELECTOR



Can't hear the weak ones? Receiver lacks sensitivity? New Model P-508 gives 20 dB gain with high selectivity to eliminate images and other out-of-band signals. Full coverage 200 KHz to 30 MHz in five bands. Continuously variable gain/attenuator control. New amplifier circuit reduces spurious outputs, improves reception.

Model P-508 \$99.95 + \$6 to ship U.S./Canada.
For 12v DC. **Model PS-90 AC adapter \$9.95.**
Sales tax in Calif.

 

Send for **FREE** catalog that shows our complete line of pre-amplifiers, antennas, baluns, converters and more.

PALOMAR ENGINEERS
Box 462222, ESCONDIDO CA 92046
Phone: (619) 747-3343
FAX: (619) 747-3346
e-mail: 75353.2175@compuserve.com